

**DEPARTMENT OF ELECTRICAL ENGINEERING**  
**NATIONAL INSTITUTE OF TECHNOLOGY, SRINAGAR**

**Exam:** Minor

**Subject –** Basic Electrical Eng (ELE-307)

**Time allowed –** 1 h 30 m

**Semester -** 3<sup>rd</sup> (CSE)

**Date :** 01-10-2018

**Max Marks –** 30

**Course Objectives:**

**CO1:** To analyze and evaluate the electrical circuits, apply basic laws in circuit theory and to determine electric circuit parameters.

**CO2:** To identify and analyze various energy sources and their transformation.

**CO3:** Power and energy relations, analysis of series parallel D.C. Circuits and network theorem along with applications.

**Note:** Attempt all questions.

**Q1: a)** The total current drawn by a circuit consisting of three resistors connected in parallel is 12 A. The voltage drop across the first resistor is 12 V, the value of second resistor is  $3\ \Omega$  and the power dissipation of the third resistor is 24 W. What are the resistances of the first and third resistors? (5)(CO1)

**b)** In Fig 1 below, find the current ( $I_3$ ) through  $4\ \Omega$  Resistor. (5)(CO1)

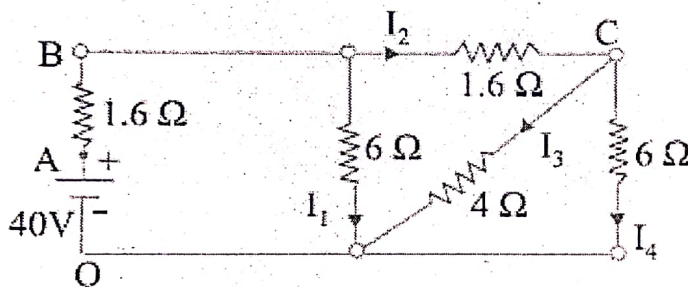


Fig 1

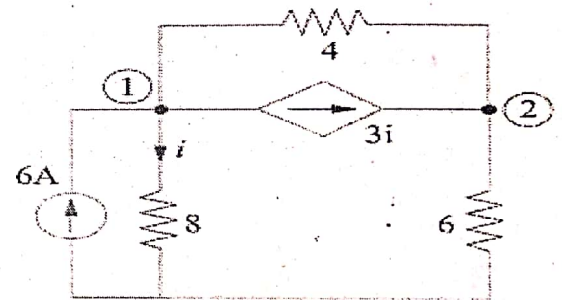


Fig 2

**Q2: a)** Define with VI-relationship the following:

I. Ideal and Practical Voltage Source

II. Ideal and Practical Current Source

(5) (CO2)

**b)** Use Nodal analysis to determine the value of current  $i$  in the network of Fig. 2. (5)(CO1)

**Q3:** Find current  $I$  in the circuit shown in Fig.3 using

I. Superposition theorem

II. Thevenin's Theorem. All resistances are in ohms.

(5,5) (CO3)

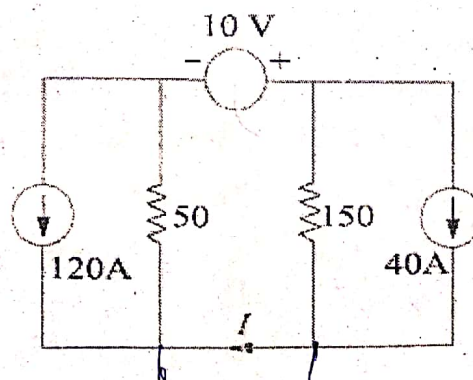


Fig 3