



*Department of Electronics and Communication*  
**NATIONAL INSTITUTE OF TECHNOLOGY SRINAGAR**  
**MAJOR EXAMINATION**

**Course: Digital Electronics and Logic Design**  
**Semester: 4<sup>th</sup> (CSE)**  
**Date: 11/06/19**

**Time: 3 hours**  
**Max Marks: 60**  
**Code: ECE-403**

**Note: Attempt any 4 questions and draw diagrams wherever necessary.**

- Q1. (a) What are the ways to represent signed numbers? Explain with examples. [5]  
(b) Apart from Hamming codes how is parity used for error detection and correction? [5]  
Explain with an example.  
(c) How do we convert binary codes to gray codes? What are the properties of gray codes. [5]  
Give its application.
- Q2. (a) Explain working of a multiplexer. Give its applications. How are they cascaded? [5]  
(b) Implement the following function using: [5]  
 $F(A,B,C,D) = \Sigma_m(2,3,6,7,8,12,14,15)$   
1. 8:1 MUX  
2. 4:1 MUX  
(c) Explain ring counter along with its logic diagram, truth table and timing diagram. [5]
- Q3. (a) Design a 3-bit asynchronous up- down counter using positive edge triggered JK- [7.5]  
flipflops. Explain its working.  
(b) Design a 4-bit synchronous odd counter using negative edge triggered D-flipflops. [7.5]  
Explain its working as well.
- Q4. Implement 4 bit binary to gray code convertor using: [15]  
a) PROM  
b) PLA  
c) PAL  
Explain the distinction between them.
- Q5. (a) Design a sequence detector that detects 10010 using moore model. [7.5]  
(b) Explain the working of Successive Approximation type ADC in detail. [7.5]

--End of Paper--