

**Department Of Electrical Engineering**  
**National Institute Of Technology Srinagar**

|                                 |                              |              |           |         |          |
|---------------------------------|------------------------------|--------------|-----------|---------|----------|
| Exam Semester                   | Course Title                 | Subject Code | Max Marks | Time    | Date     |
| Major B.Tech (3 <sup>rd</sup> ) | Basic Electrical Engineering | ELE-307      | 60        | 3 hours | 24-11-18 |

**Course Objectives:**

- CO1 :** To analyse and evaluate the electrical circuits, apply basic laws in circuit theory and to determine electric circuit parameters.
- CO2 :** Power and energy relations, analysis of series parallel D.C. Circuits and network theorem along with applications.
- CO3 :** Analysis of A.C circuits, network theorems in A.C circuits and understanding the concept of active and reactive power, resonance.
- CO4 :** To study the characteristics of 3 phase systems, Current and voltage relations in star/delta configuration's, Balanced / un-balanced systems.
- CO5 :** To study the basic operation of transformer and laws of electromagnetic induction

**Note: Attempt any 4 questions**

**Q1: a)** Find the current 'i' in Fig 1

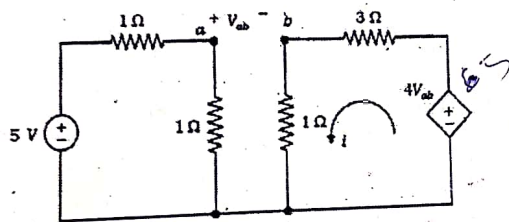


Fig 1

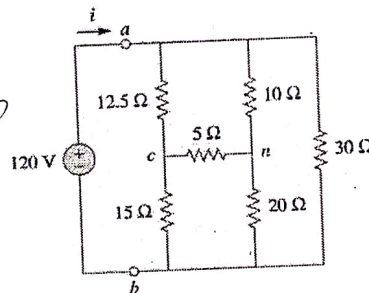


Fig 2

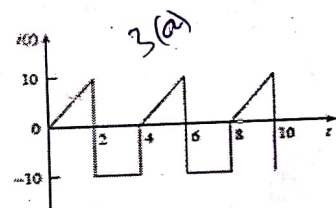


Fig 3

**b)** Obtain the equivalent resistance  $R_{ab}$  for the circuit in Fig 2 and use it to find the current i. (CO2) (8)

**Q2: a)** In Fig 4, Find the Thevenin's equivalent Circuit with respect to terminals a and b. (CO2) (8)

**b)** Find the value of maximum power that can be transferred across  $R_L$  using Maximum Power Transfer Theorem for Fig 5 (CO3) (7)

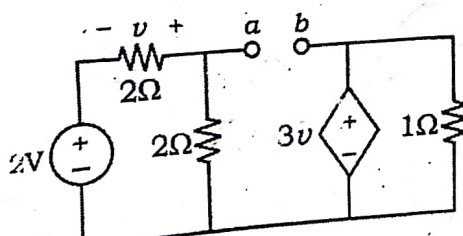


Fig 4

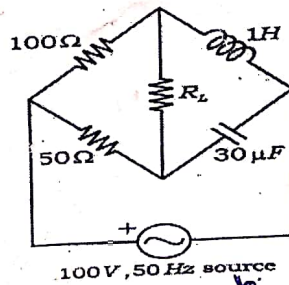


Fig 5

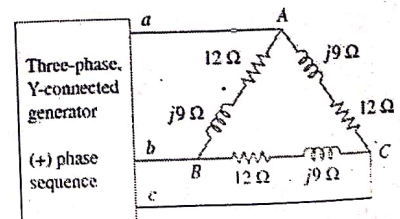


Fig 6

**Q3: a)** Find the average and effective values of the current waveform of Figure 3. If the current is passed through a 2-Ω resistor, find the power absorbed by the resistor (CO2) (7)

**b)** Calculate all the phase and line currents in the Fig 6, if  $V_{an} = 220 \cos(\omega t + 60^\circ)$  (CO4) (8)

**Q4: a)** If a series RLC circuit is excited by a voltage source of  $10 \sin \omega t$ , given  $R = 8K\Omega$ ,  $L = 0.2mH$ ,  $C = 8\mu F$ , find

- (1) Resonant frequency ( $\omega_r$ ),
- (2) Quality factor (Q),
- (3) Bandwidth (B.W)

(CO3) (6)

**b)** For a series RLC circuit excited by an ac voltage source, draw the following characteristics showing inductive and capacitive regions.

- (1)  $Z$  vs  $\omega$
- (2)  $I$  vs  $\omega$
- (3) power factor angle vs  $\omega$
- (4)  $X$  vs  $\omega$

(CO3) (9)

(CO5) (9)

**Q5: a)** Explain (briefly) following with respect to Magnetic Circuits

- 1) Self Inductance
- 2) Mutual Inductance
- 3) Coefficient of mutual coupling

(CO5) (6)

**b)** Explain the basic principle of operation of a transformer.